

# Assignment-1

Date	10 September 2022
Team ID	PNT2022TMID31899
Student Register Number	721219106055
Maximum Marks	2 Marks

## Question-1:


Make a Common Circuit in tinkercad using PIR sensor ,Buzzer and LED. Motion detect by sensor and make alarm.

### Solution:

```
void setup()
{
    pinMode(LED_BUILTIN, OUTPUT);
}

void loop()
{
    digitalWrite(LED_BUILTIN, HIGH);
    delay(1000);      // Wait for 1000 millisecond(s)
    digitalWrite(LED_BUILTIN, LOW);
    delay(1000);      // Wait for 1000 millisecond(s)
}
```

### Circuit Diagram:

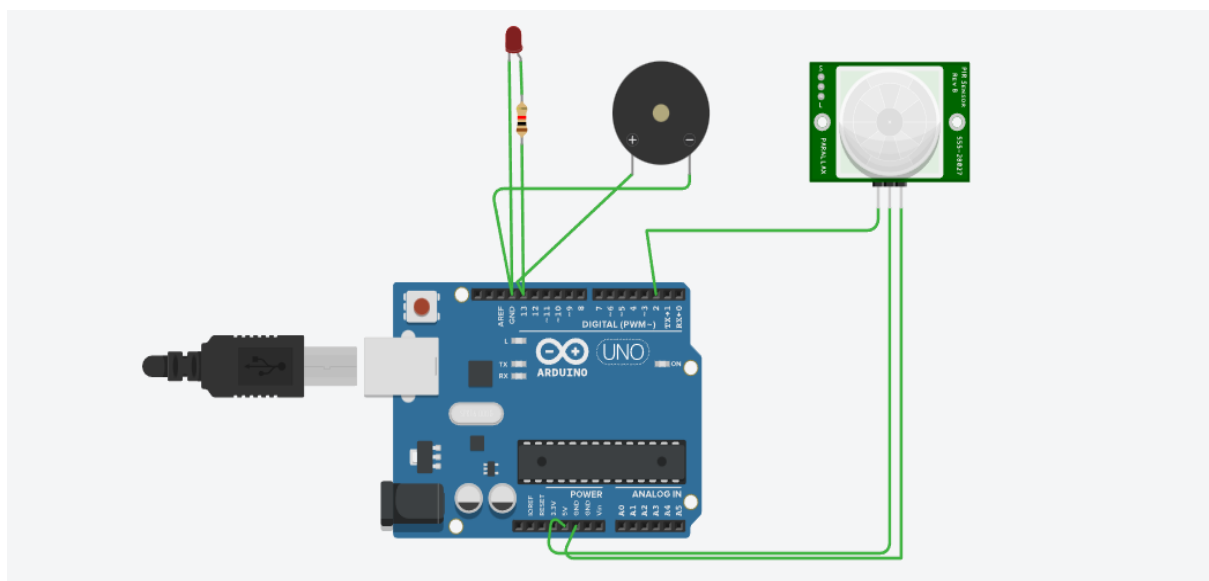

### **Components:**

S.No	Name	Quantity	Component
1.	U1	1	Arduino Uno R3
2.	PIEZO1	1	Piezo
3.	PIR1	1	PIR Sensor
4.	R1	1	Resistor
5.	D1	1	Red LED